

## Assignment-2

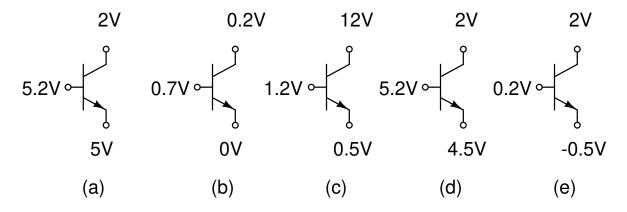1. For the following npn BJT, determinte the region of operation: Cut-off, active or saturation. Given:  $V_{BE(on)} = 0.7$  V and  $V_{CE(sat)} = 0.3$  V.




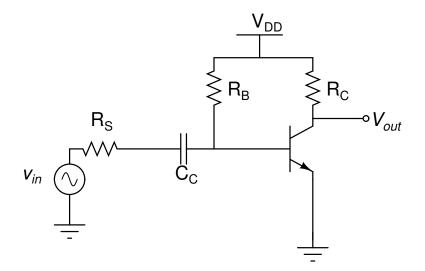2. For the following self biased CE amplifier, find the DC operating points ( $I_B$ ,  $I_C$  and  $V_{CE}$ ). Draw the small signal circuit of it and find the expression of the gain of the amplifier and also calculate its value. Given:  $R_B$  =465 k $\Omega$ ,  $R_C$ =2.5 k $\Omega$   $V_{DD}$ =10 V,  $V_{BE(on)}$  = 0.7 V,  $\beta$  = 100 and  $V_{CE(sat)}$  = 0.3 V.



IIT BBS 1

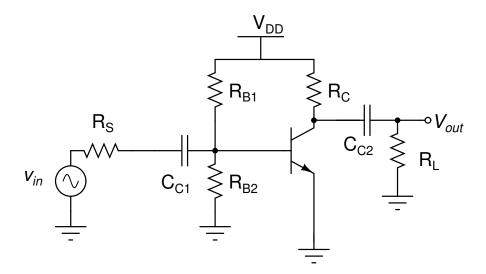3. For the following resistive divider based CE amplifier, find the expression of the gain of the amplifier and also calculate its value. Given:  $R_{B1}$  =206 k $\Omega$ ,  $R_{B2}$  =20 k $\Omega$ ,  $R_{C}$ =  $R_{L}$ = $R_{S}$ =2 k $\Omega$   $V_{DD}$ =10 V,  $V_{BE(on)}$  = 0.7 V,  $\beta$  = 200 and  $V_{CE(sat)}$  = 0.3 V.



IIT BBS 2